

Sc!ence


Name:		()
-------	--	---	---

Class:

Date: / /

Resistors in Series and Parallel - Advanced

Question One:

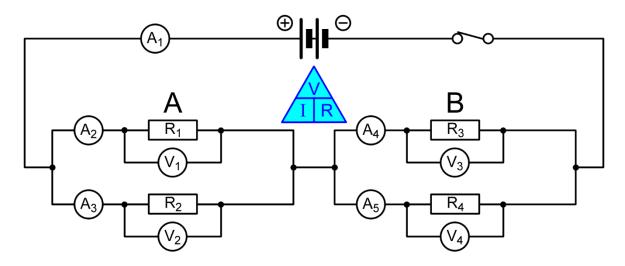


Battery = 15 V $R_1 = 20 \Omega$ $R_2 = 50 \Omega$ $R_3 = 40 \Omega$ $R_4 = 80 \Omega$

- (a) Calculate the resistance through part **A** and part **B** of the circuit, and hence calculate the total resistance through the circuit, *i.e.* the value for R_e.
- **(b)** Calculate the current through the main circuit, *i.e.* the value on A₁.
- (c) Calculate the potential difference across part A and across part B of the circuit.
- (d) Calculate the current across R₁, R₂, R₃ and R₄, *i.e.* the readings on A₂, A₃, A₄ and A₅.

 	• • • • • • • • • • • • • • • • • • • •	

Question Two:

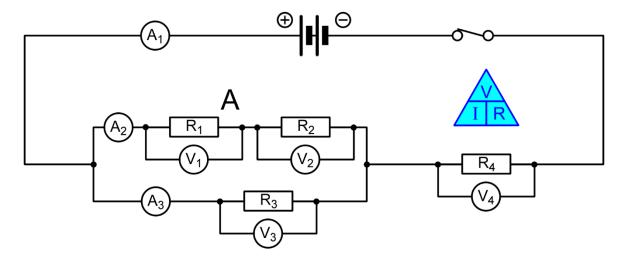

Battery = 18 V $R_1 = 20 \Omega$ $R_2 = 30 \Omega$ $R_3 = 100 \Omega$ $R_4 = 40 \Omega$

- (a) Calculate the resistance through part **A** of the circuit, and hence calculate the total resistance through the circuit, *i.e.* the value for R_e.
- (b) Calculate the current through the main circuit, i.e. the value on A₁.
- (c) Calculate the potential difference across part ${\bf A}$ of the circuit and across R_4 , *i.e.* the value on V_4

(d)	Calculate the current across R ₁ , R ₂ , and R ₃ <i>i.e.</i> the readings on A ₂ and A ₃ .

• Scan the QR code below for the answers to this assignment.



http://www.nygh.sg/lower_secondary_science/sec_two_science/sec_two_physics/resistors_advanced_answers.pdf