

Science


Name: ()

Class:

Date: / /

Resistors in Series and Parallel – Introduction

Question 1 – Resistors in Series:

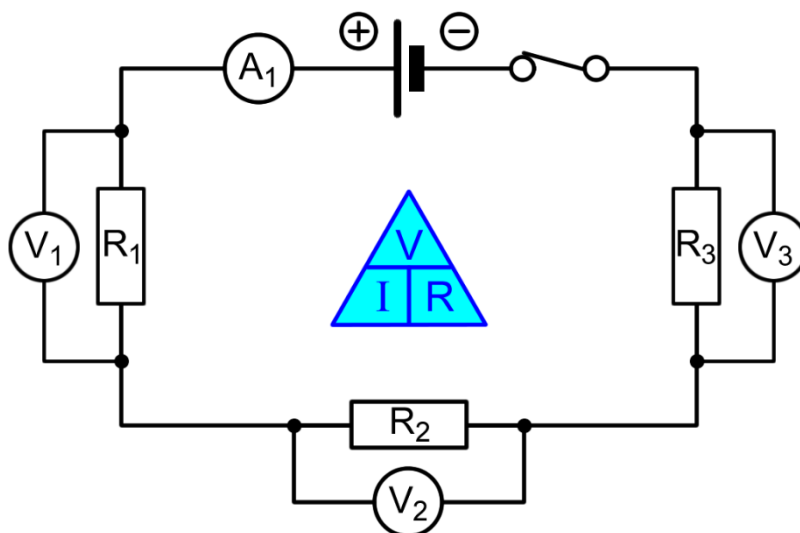

- Battery = 12 V
- $R_1 = 20 \Omega$
- $R_2 = 50 \Omega$
- $R_3 = 80 \Omega$

Ohm's Law: $V = I \times R$

Effective resistance of circuit = sum of resistors in series: $R_e = R_1 + R_2 + R_3$

All resistors (components) in a series circuit have the same current (I) flowing through them

The potential difference (V) splits between the resistors (components) in a series circuit

So, for the above parallel circuit, e.m.f. of battery = $V_1 + V_2 + V_3$

- Calculate the effective resistance, R_e , of the circuit.
- Calculate the current flowing through the circuit, *i.e.* the reading on A_1 .
- Calculate the potential difference across R_1 , R_2 and R_3 , *i.e.* the readings on V_1 , V_2 and V_3 .

.....

.....

.....

.....

.....

.....


.....

.....

.....

.....

Question Two – Resistors in Parallel

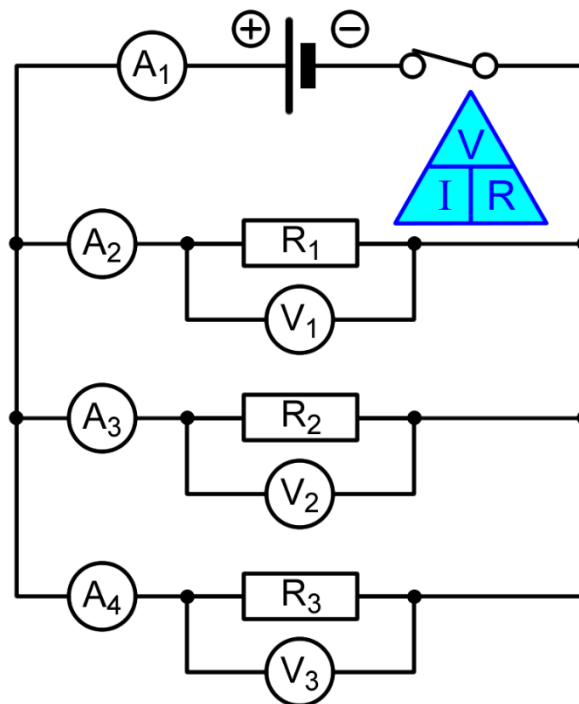

- Battery = 12 V • $R_1 = 20\ \Omega$ • $R_2 = 50\ \Omega$ • $R_3 = 80\ \Omega$

Ohm's Law: $V = I \times R$

Effective resistance of a parallel circuit: $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$


The current (I) splits between the resistors (components) in a parallel circuit

So, for the above parallel circuit, reading on $A_1 = A_2 + A_3 + A_4$

All resistors (components) in a parallel circuit have the same potential difference (V) across them

- Calculate the effective resistance, R_e , of the circuit.
- Calculate the current flowing through the circuit, *i.e.* the reading on A_1 .
- State the potential difference across R_1 , R_2 and R_3 , *i.e.* the readings on V_1 , V_2 and V_3 .
- Calculate the current across R_1 , R_2 and R_3 , *i.e.* the readings on A_1 , A_2 and A_3 .

Question Three – Resistors in Parallel

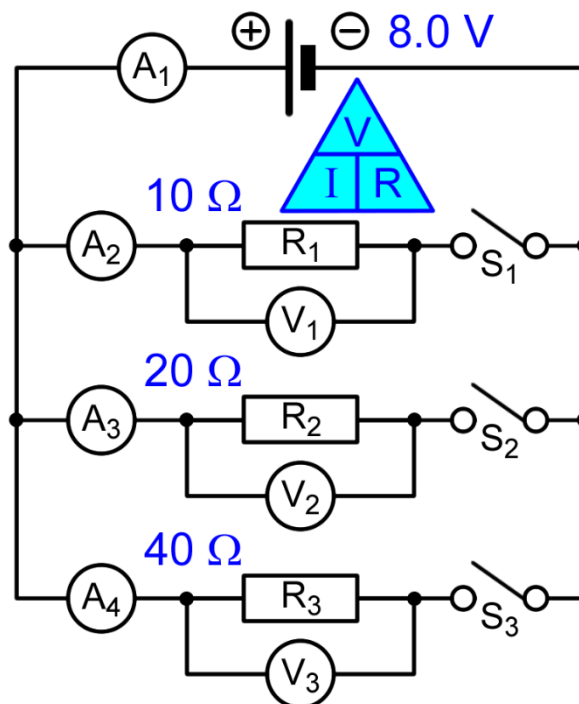

- Battery = 8.0 V • $R_1 = 10\ \Omega$ • $R_2 = 20\ \Omega$ • $R_3 = 40\ \Omega$

Ohm's Law: $V = I \times R$

Effective resistance of a parallel circuit: $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

The current (I) splits between the resistors (components) in a parallel circuit

So, for the above parallel circuit, reading on $A_1 = A_2 + A_3 + A_4$

All resistors (components) in a parallel circuit have the same potential difference (V) across them

- (a) Calculate the current through the main circuit (reading on A_1) when only switch S_1 is closed.
- (b) (i) Calculate the effective resistance through the circuit when only switch S_1 and switch S_2 are closed.
- (ii) Calculate the current through the main circuit (reading on A_1) when only switch S_1 and switch S_2 are closed.
- (c) (i) Calculate the effective resistance through the circuit when switch S_1 , switch S_2 and switch S_3 are all closed.
- (ii) Calculate the current through the main circuit (reading on A_1) when switch S_1 , switch S_2 and switch S_3 are all closed.
- (d) Calculate the readings on A_2 , A_3 , A_4 when switch S_1 , switch S_2 and switch S_3 are all closed.
- (e) How does the effective resistance of the circuit, R_e , change as the switches are closed and the number of resistors in parallel increases?
- (f) How does the current through the main circuit (reading on A_1) change as the switches are closed and the number of resistors in parallel increases?

This image shows a full page of white paper with horizontal dotted lines. The lines are evenly spaced and run across the width of the page, providing a guide for handwriting practice. There are no margins, text, or other markings on the page.

- Scan the QR code below for the answers to this assignment.



http://www.nygh.sg/lower_secondary_science/sec_two_science/sec_two_physics/resistors_introduction_answers.pdf