

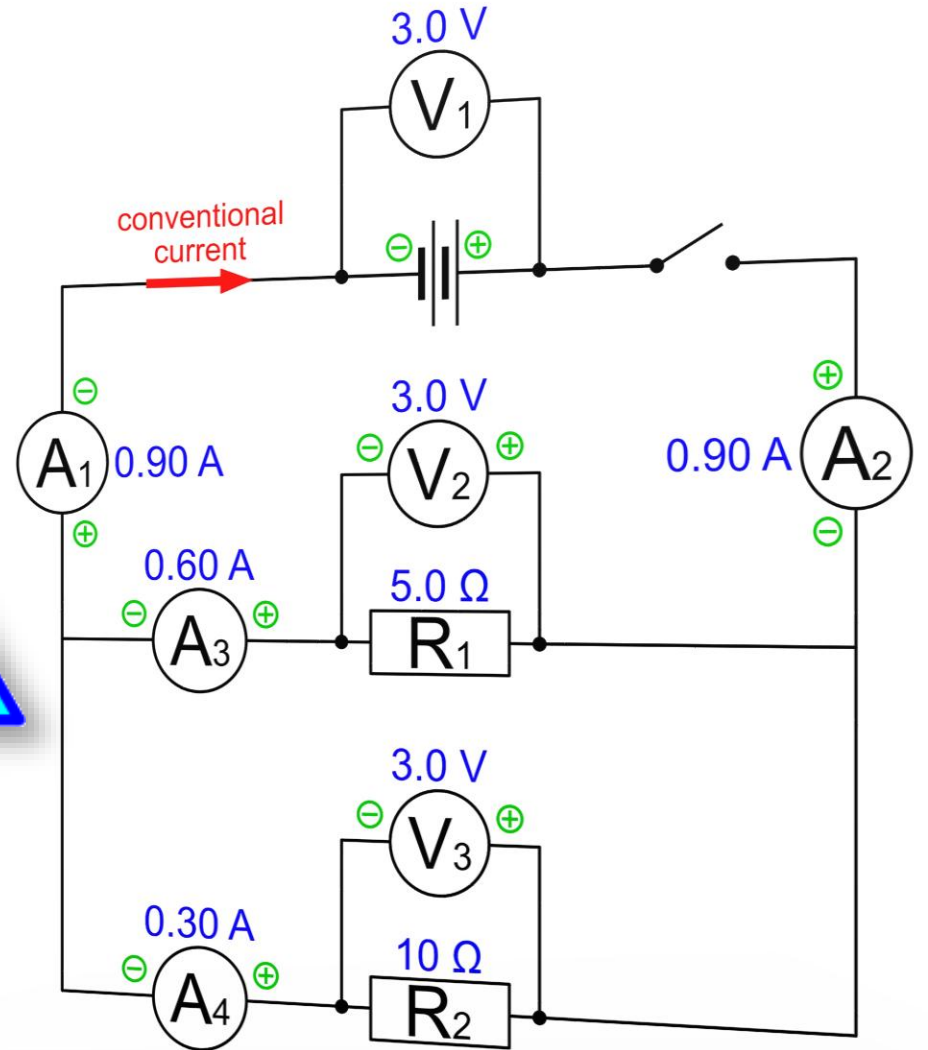


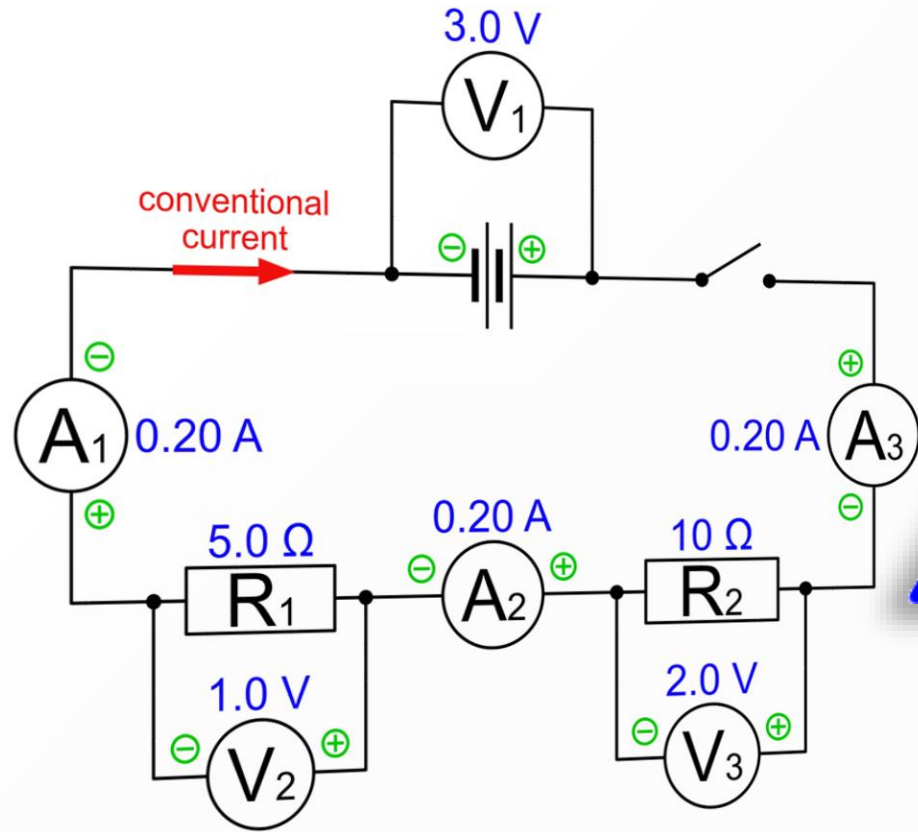A Summary of Series and Parallel Circuits



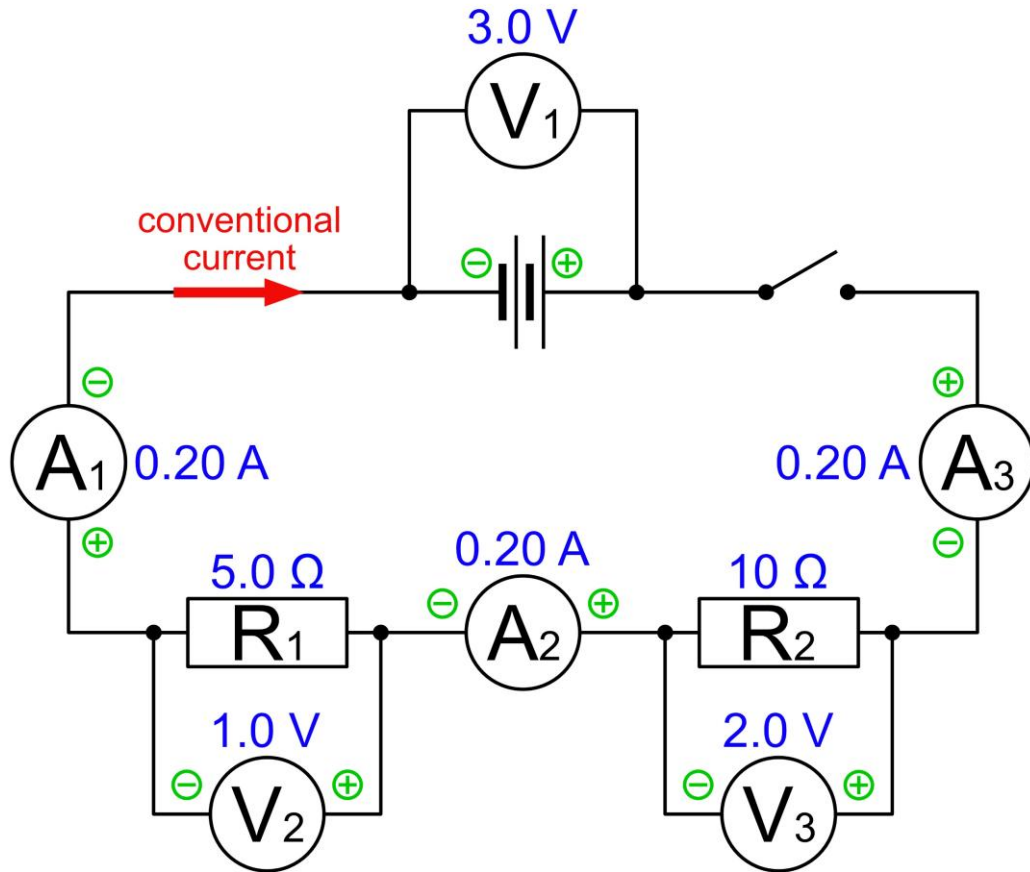

A Summary of Series and Parallel Circuits




General Rules for a Series Circuit:

- The current is the same at all points in the circuit.
i.e. $A_1 = A_2 = A_3$
- The sum of the potential differences (p.d.) across the resistors equals the electromotive force (e.m.f.) of the battery.
i.e. $V_1 = V_2 + V_3$
- The effective resistance (R_e) through the circuit equals the sum of the resistors.
i.e. $R_e = R_1 + R_2$
- If an additional resistor, R_3 , is introduced in series, then the effective resistance (R_e) will *increase* ($R_e = R_1 + R_2 + R_3$) while the current through the circuit will *decrease* ($I = V/R_e$).



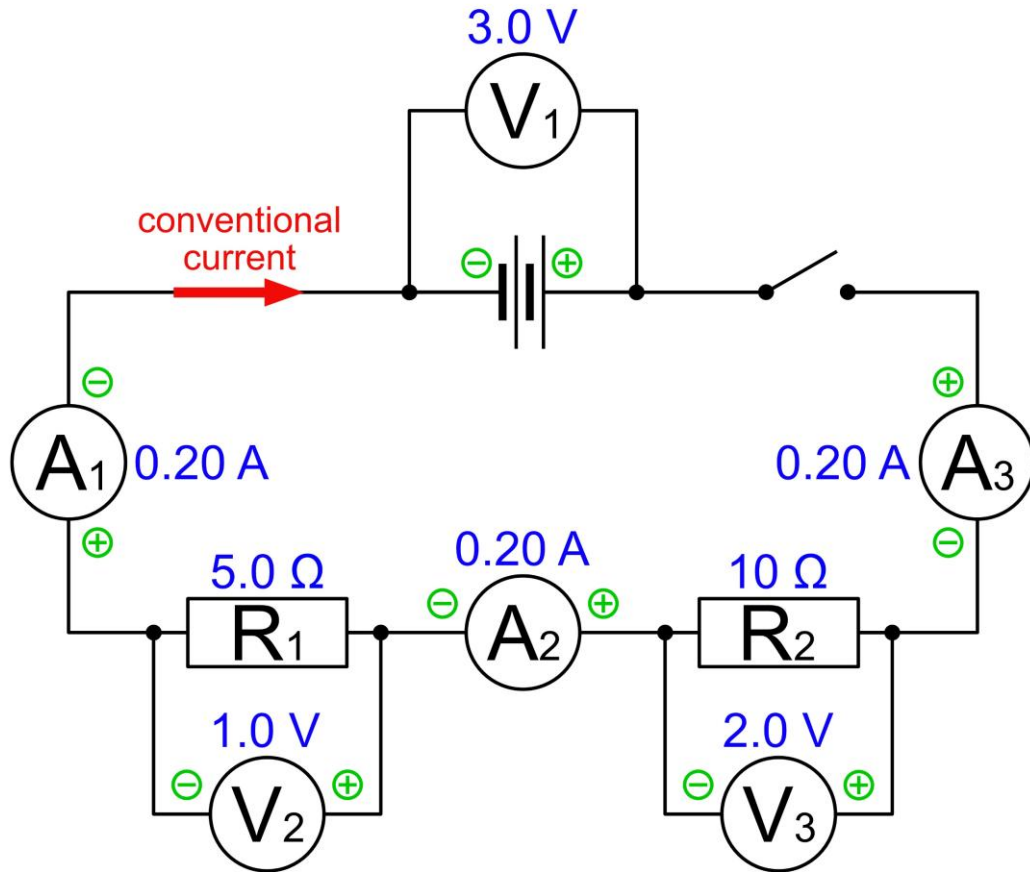A Summary of Series and Parallel Circuits




Calculations for this Circuit:

- effective resistance = $R_e = R_1 + R_2$
 $R_e = 5.0 \, \Omega + 10 \, \Omega = 15 \, \Omega$
- current through circuit (readings on A_1 , A_2 and A_3)
 $I = V/R = 3.0 \, \text{V} / 15 \, \Omega = 0.20 \, \text{A}$
- potential difference across R_1 (reading on V_2)
 $V_2 = I \times R_1 = 0.20 \, \text{A} \times 5.0 \, \Omega = 1.0 \, \text{V}$
- potential difference across R_2 (reading on V_3)
 $V_3 = I \times R_2 = 0.20 \, \text{A} \times 10 \, \Omega = 2.0 \, \text{V}$
- **Note:** The sum of the potential differences across the two resistors, R_1 and R_2 , equals the electromotive force of the battery.
i.e. $1.0 \, \text{V} + 2.0 \, \text{V} = 3.0 \, \text{V}$



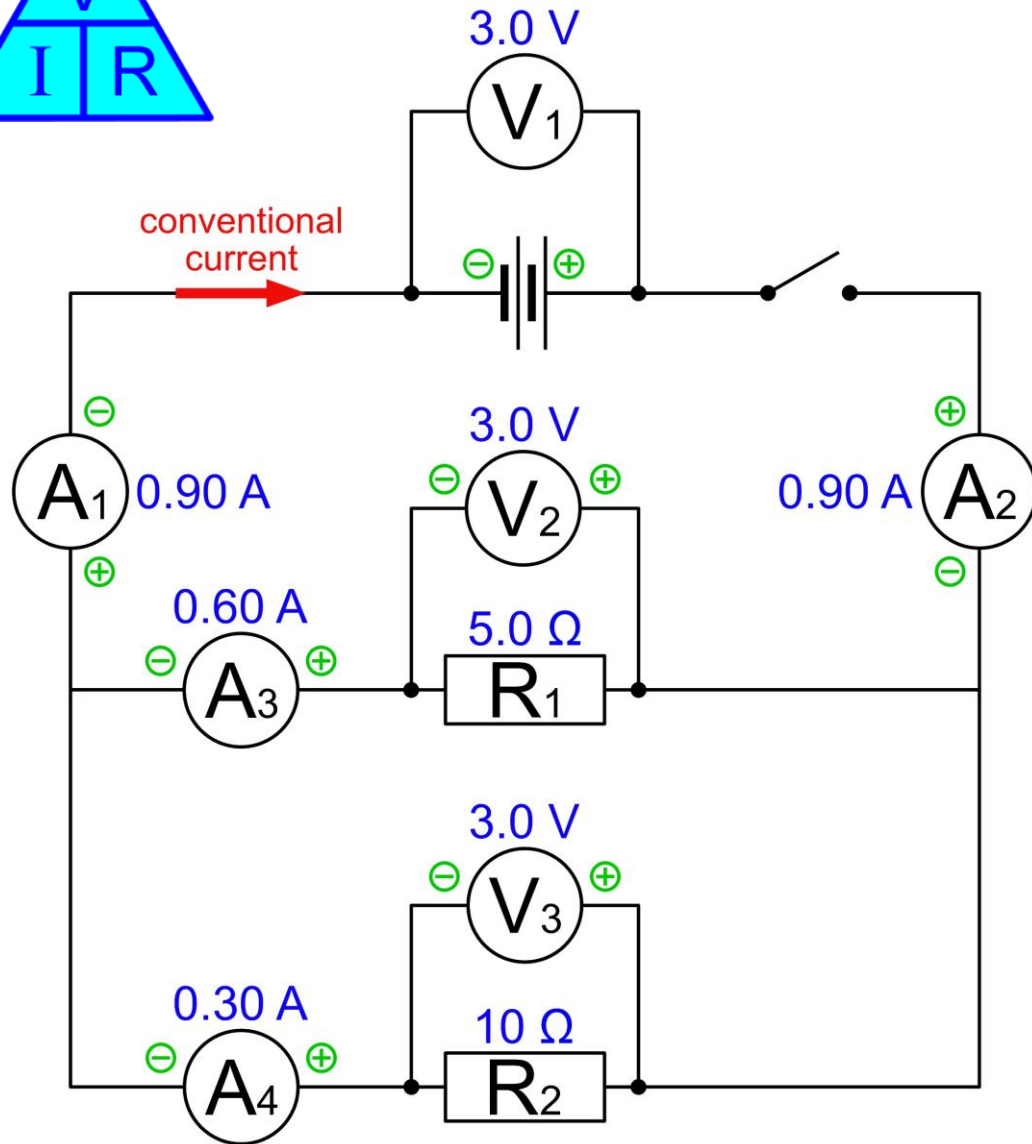A Summary of Series and Parallel Circuits



General Rules for a Parallel Circuit:

- The current divides to flow through both resistors. The current through the main circuit equals the sum of the currents through the branches of the circuit.

$$i.e. A_1 = A_2 = A_3 + A_4$$

- The potential difference (p.d.) through the individual resistors is the same as the electromotive force (e.m.f.) of the battery.

$$i.e. V_1 = V_2 = V_3$$

- The effective resistance (R_e) through the circuit is given by the equation: $1/R_e = 1/R_1 + 1/R_2$


- If an additional resistor, R_3 , is introduced in parallel, then the effective resistance (R_e) will *decrease* ($1/R_e = 1/R_1 + 1/R_2 + 1/R_3$) while the current through the main circuit (A_1 and A_2) will *increase* ($I = V/R_e$).

- Note:** The effective resistance (R_e) is *smaller* than value of the *smallest resistor* in the parallel circuit.

$$i.e. \text{ if } R_1 < R_2, \text{ then } R_e < R_1$$



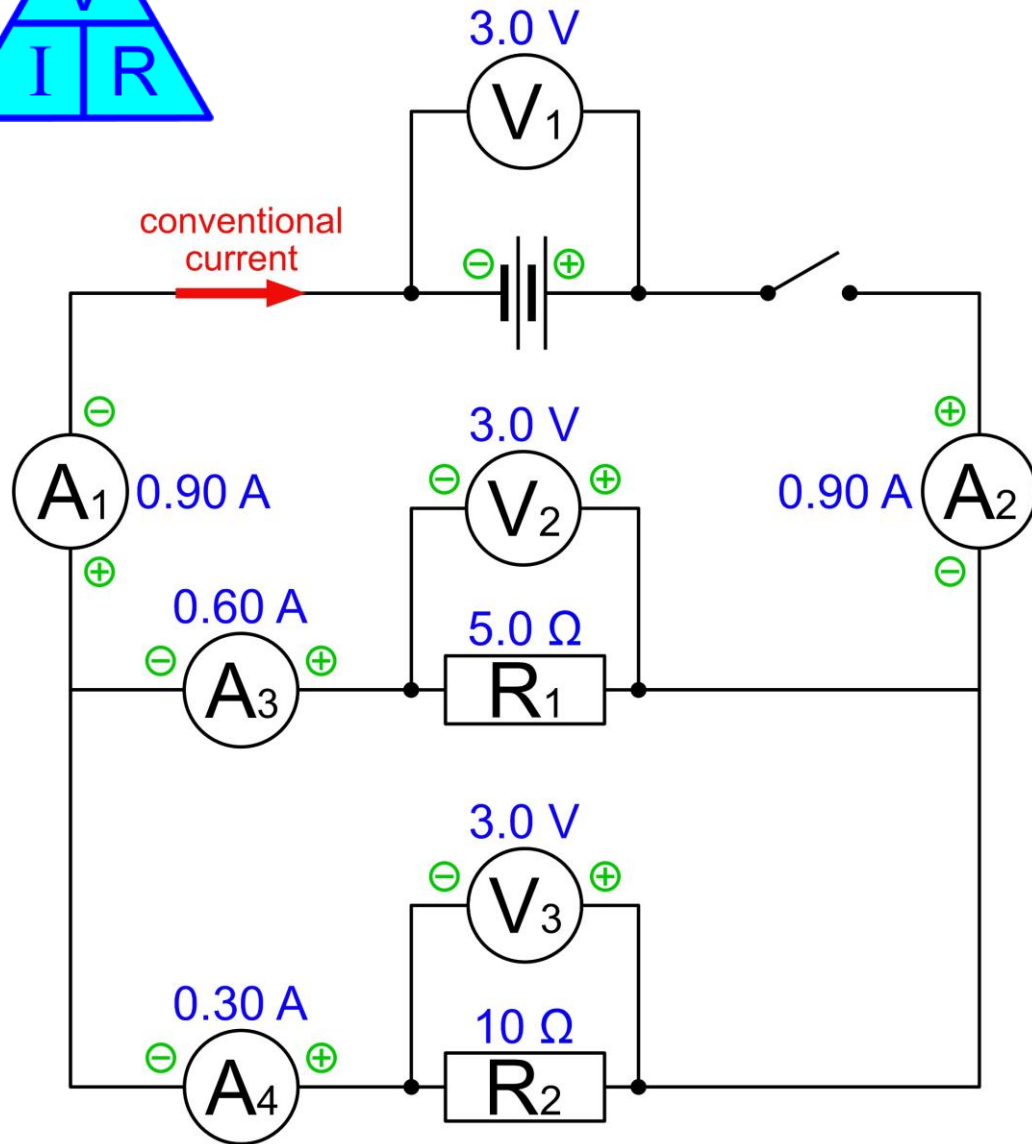A Summary of Series and Parallel Circuits



Calculations for this Circuit:

- effective resistance = $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$

$$\frac{1}{R_e} = \frac{1}{5.0 \Omega} + \frac{1}{10 \Omega}$$

$$\frac{1}{R_e} = 0.20 + 0.10$$

$$\frac{1}{R_e} = 0.30$$

$$R_e = \frac{1}{0.30}$$

$$R_e = 3.33 \Omega \text{ or } 3.3 \Omega \text{ to 2 s.f.}$$

- potential difference across R_1 (reading on V_2) and R_2 (reading on V_3)

$$V_1 = V_2 = V_3 \text{ so } V_2 = 3.0 \text{ V and } V_3 = 3.0 \text{ V}$$

- current through main circuit (readings on A_1 and A_2)

$$I = \frac{V}{R} = \frac{3.0 \text{ V}}{3.33 \Omega} = 0.90 \text{ A}$$


- current through $A_3 = I = \frac{V_2}{R_1} = \frac{3.0 \text{ V}}{5.0 \Omega} = 0.60 \text{ A}$

- current through $A_4 = I = \frac{V_3}{R_2} = \frac{3.0 \text{ V}}{10 \Omega} = 0.30 \text{ A}$

- Note:** $A_3 + A_4 = 0.6 \text{ A} + 0.3 \text{ A} = 0.90 \text{ A}$

which is the current through the main circuit, A_1 & A_2

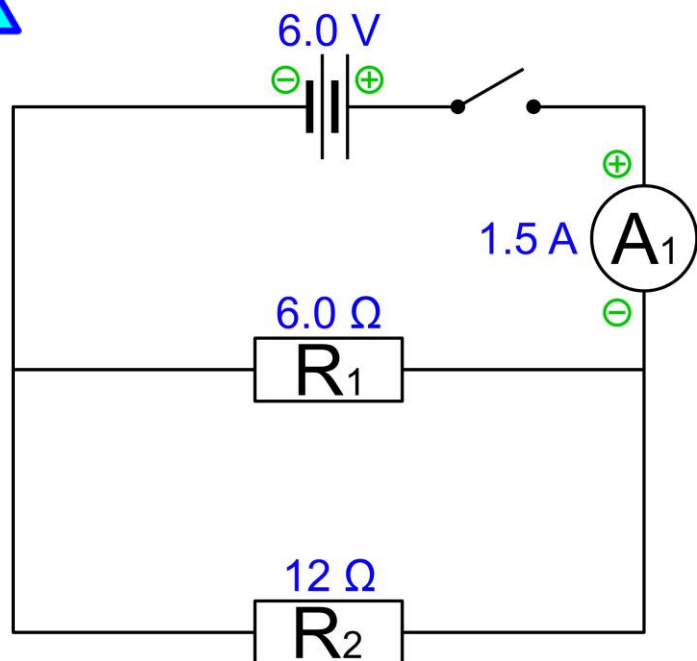A Summary of Series and Parallel Circuits




Circuit A

Important to Note #1:

- For a parallel circuit, the value of the effective resistance, R_e , is *always smaller* than the value of the smallest resistor.

For circuit A:
 $4.0 \Omega < 6.0 \Omega$

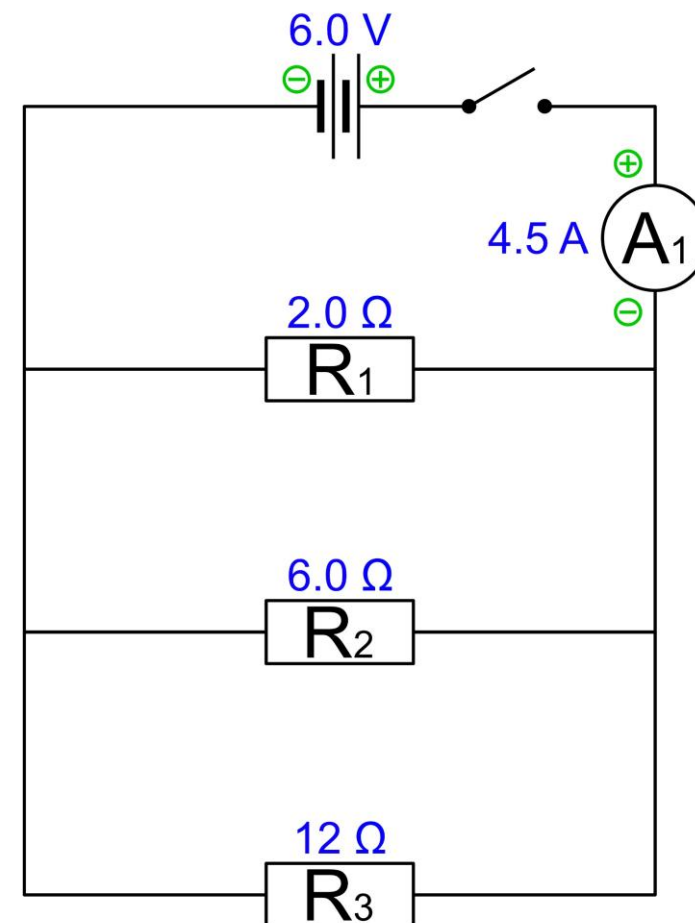For circuit B:
 $1.3 \Omega < 2.0 \Omega$



Circuit B


- effective resistance = $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$
 $\frac{1}{R_e} = \frac{1}{6.0 \Omega} + \frac{1}{12 \Omega}$
 $\frac{1}{R_e} = 0.167 + 0.083$
 $\frac{1}{R_e} = 0.25$
 $R_e = \frac{1}{0.25}$
 $R_e = 4.0 \Omega$ to 2 s.f.

- effective resistance = $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
 $\frac{1}{R_e} = \frac{1}{2.0 \Omega} + \frac{1}{6.0 \Omega} + \frac{1}{12 \Omega}$
 $\frac{1}{R_e} = 0.50 + 0.167 + 0.083$
 $\frac{1}{R_e} = 0.75$
 $R_e = \frac{1}{0.75}$
 $R_e = 1.33 \Omega$ or 1.3Ω to 2 s.f.

A Summary of Series and Parallel Circuits



Circuit A

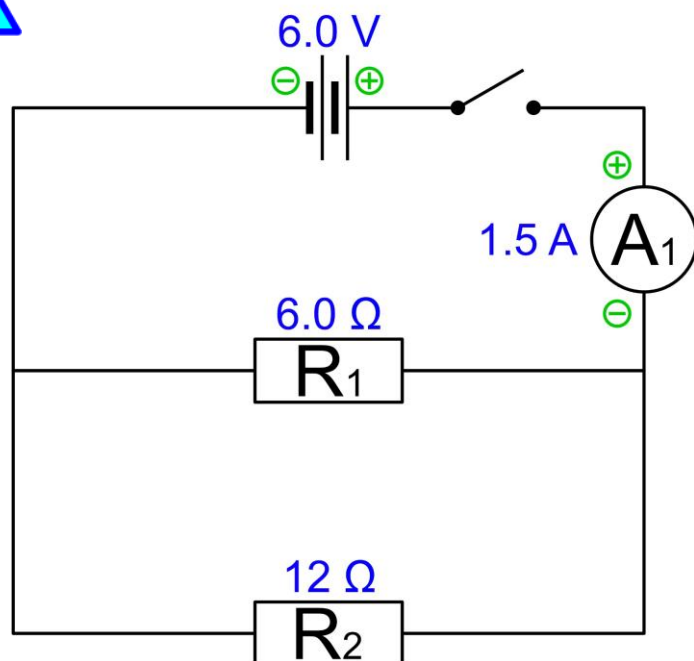

- effective resistance = $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$
 $\frac{1}{R_e} = \frac{1}{6.0\ \Omega} + \frac{1}{12\ \Omega}$
 $\frac{1}{R_e} = 0.167 + 0.083$
 $\frac{1}{R_e} = 0.25$
 $R_e = \frac{1}{0.25}$
 $R_e = 4.0\ \Omega$ to 2 s.f.

Important to Note #2:

- Introducing a new resistor in parallel will *reduce* the value of the effective resistance, R_e , of the circuit, and hence *increase* the current through the main circuit.

For circuit A:

$$R_e = 4.0\ \Omega$$

For circuit B:

$$R_e = 1.3\ \Omega$$


For circuit A:

Current = 1.5 A

For circuit B:

Current = 4.5 A

Circuit B

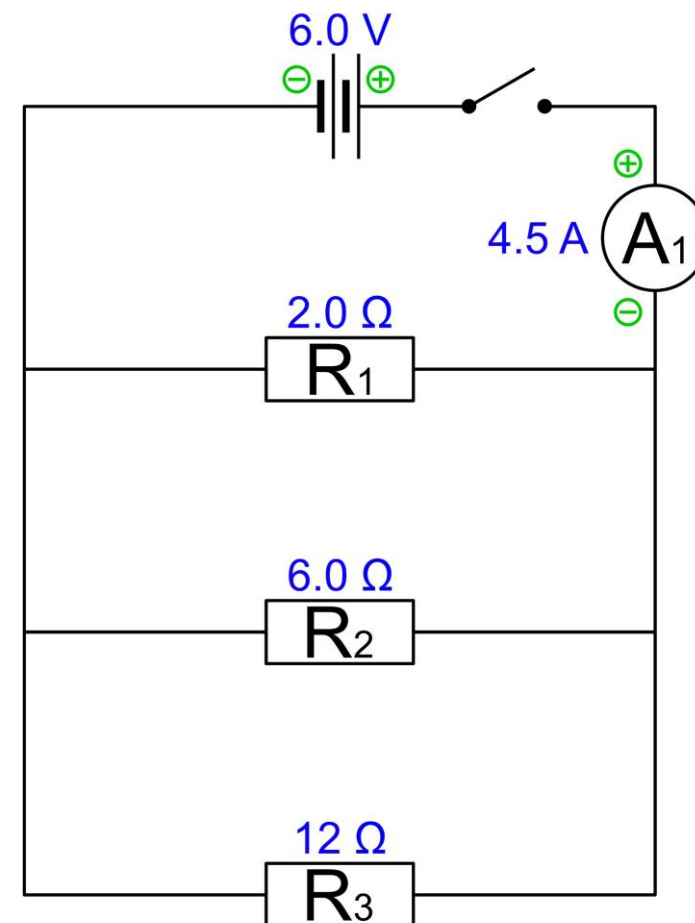

- effective resistance = $\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
 $\frac{1}{R_e} = \frac{1}{2.0\ \Omega} + \frac{1}{6.0\ \Omega} + \frac{1}{12\ \Omega}$
 $\frac{1}{R_e} = 0.50 + 0.167 + 0.083$
 $\frac{1}{R_e} = 0.75$
 $R_e = \frac{1}{0.75}$
 $R_e = 1.33\ \Omega$ or $1.3\ \Omega$ to 2 s.f.